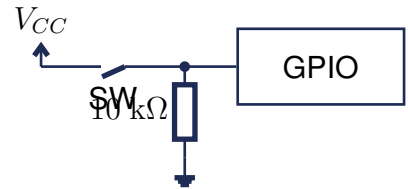


Floating input: incorrect




No defined voltage; noise can change the reading

External pull-down




Open = 0; pressed = 1

External pull-up

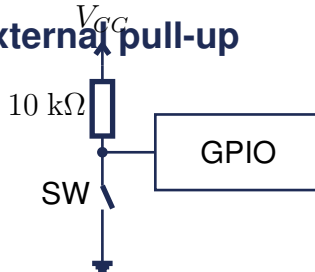


Open = 1; pressed = 0

Active-low input

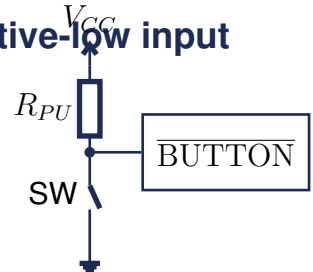


Pressed is the active state at logic 0

Internal pull-up

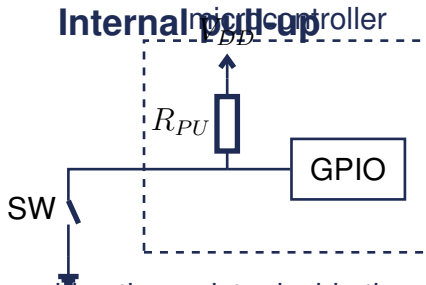


Software enables the resistor inside the device

RC hardware debounce

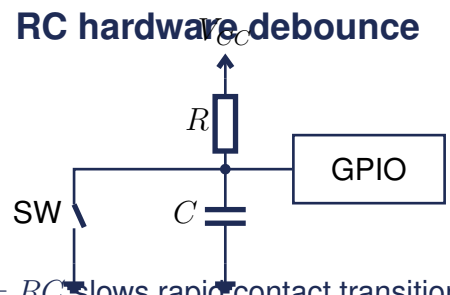


RC slows rapid contact transitions

Protected digital input

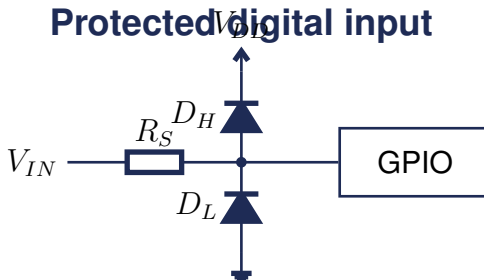

Series resistance and clamps limit abnormal input current

Switch driving a logic input

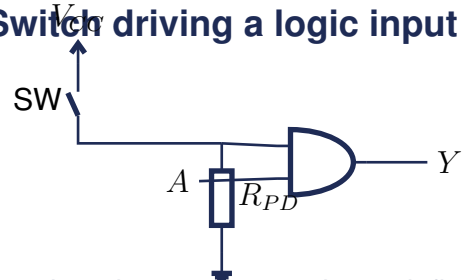

The resistor keeps the gate input defined