
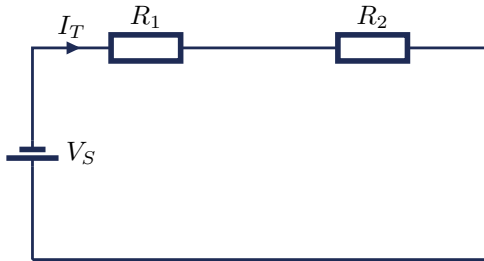


Series: one path

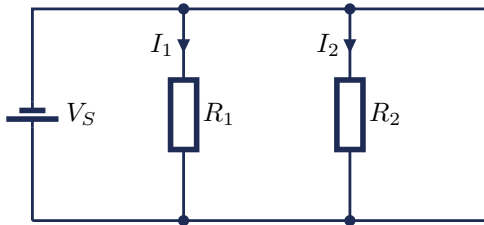

Same current through
both resistors

Parallel: two branches



Same voltage across
both branches