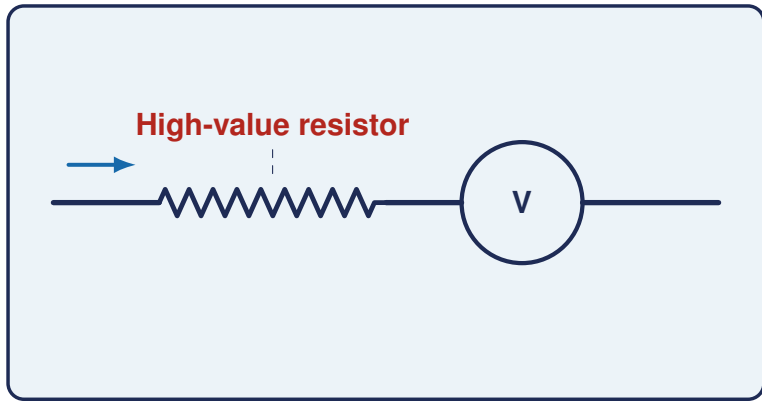


Voltmeter internal path: high resistance limits current



Connect in parallel across two points. High internal resistance keeps the meter from changing the circuit much.